


Filters


High pass RC filter (Differentiator)

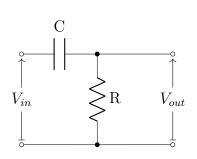

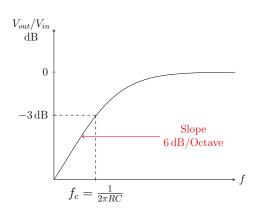



Low pass RC filter (Integrator)

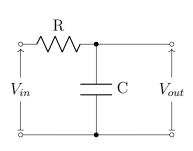

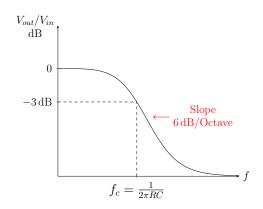


Band stop

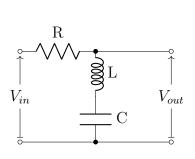


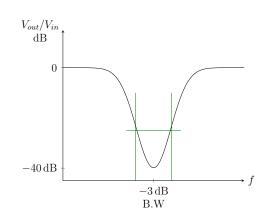

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

Band Pass

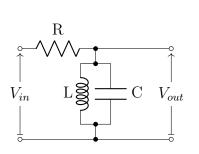

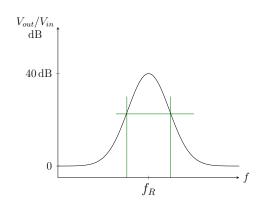

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$
$$Q = \frac{f_R}{\text{BW}}$$

Twin T notch filter

